

ANSWER SCHEME
CHAPTER 3: ELECTRIC CURRENT AND DIRECT CURRENT CIRCUITS

No.	Answer Scheme
1	(a) $V = IR$ $12 = I(6)$ $I = 2 \text{ A}$ (b) $I = \frac{Q}{t}$ $2 = \frac{Q}{2}$ $Q = 4 \text{ C}$
2	(a) $I = \frac{Q}{t}$ $I = \frac{Ne}{t}$ $5 = \frac{N(1.60 \times 10^{-19})}{5}$ $N = 1.56 \times 10^{20} \text{ electrons}$ (b) $Q = It$ $= (5)(10)$ $= 50 \text{ C}$
3	$R = \frac{\rho l}{A}$ $= \frac{(2.82 \times 10^{-8})(15000)}{5.0 \times 10^{-4}}$ $= 0.846 \, \Omega$
4	$R = \frac{V}{I}$ $= \frac{1.5}{1200}$ $= 1.25 \times 10^{-3} \, \Omega$ $R = \frac{\rho l}{A}$ $1.25 \times 10^{-3} = \frac{(1.72 \times 10^{-8})(0.32)}{\pi r^2}$ $r = 1.18 \times 10^{-3} \text{ m}$
5	$l = \frac{RA}{\rho}$

	$= \frac{(1)[\pi(0.5 \times 10^{-3})^2]}{3.5 \times 10^{-5}}$ $= 0.022 \text{ m}$
6	$R_{\text{eff}} = R_1 + R_2 + R_3$ $= 5 + 10 + 15$ $= 30 \Omega$
7	$\frac{1}{R_{\text{eff}}} = \frac{1}{4} + \frac{1}{6}$ $R_{\text{eff}} = 2.4 \Omega$
8	Parallel: $\frac{1}{R_{23}} = \frac{1}{4} + \frac{1}{8}$ $R_{23} = 2.67 \Omega$ $R_{\text{eff}} = R_1 + R_{23} + R_4$ $= 3 + 2.67 + 6$ $= 11.67 \Omega$
9	$\frac{1}{R_{\text{eff}}} = \frac{1}{100} + \frac{1}{R_V}$ $R_{\text{eff}} = \frac{100R_V}{R_V + 100}$ $V = IR_{\text{eff}}$ $2.7 = (30 \times 10^{-3}) \left(\frac{100R_V}{R_V + 100} \right)$ $R_V = 900 \Omega$
10	(a) $V_1 = IR_1$ $= (1.11)(10)$ $= 11.1 \text{ V}$ (b) $V_1 + V_{23} = 15$ $11.1 + V_{23} = 15$ $V_{23} = 3.9 \text{ V}$ $V_{23} = V_2 = V_3 = 3.9 \text{ V}$