

TOPIC 3: ELECTRIC CURRENT AND DIRECT CURRENT CIRCUITS

1. A $6.0\ \Omega$ resistor is placed across the terminal of a $12.0\ \text{V}$ battery. Calculate the
 - (a) current flows through the resistor.
 - (b) magnitude of charge **passes** through the resistor in $2.0\ \text{s}$.

[2 A, 4 C]

2. A current of $5.0\ \text{A}$ flows in a copper wire for $5\ \text{s}$. Calculate the
 - (a) number of electron that flows in the wire within that time.
 - (b) amount of charge flows in the wire for $10\ \text{s}$.

[1.56×10^{20} , 50 C]

3. The aluminium wire used in the high voltage power lines has a cross sectional area of $5.0 \times 10^{-4}\ \text{m}^2$. What is the resistance of $15\ \text{km}$ of this wire?
(Given $\rho_{\text{aluminium}} = 2.82 \times 10^{-8}\ \Omega\ \text{m}$)

[0.846 Ω]

4. A cylindrical copper cable across a potential difference of $1.5\ \text{V}$ carries a current of $1200\ \text{A}$. If the length of the cable is $0.32\ \text{m}$, what is the radius of the cable?
(Given $\rho_{\text{copper}} = 1.72 \times 10^{-8}\ \Omega\ \text{m}$)

[$1.18 \times 10^{-3}\ \text{m}$]

5. A carbon wire has a resistance of $1\ \Omega$ and a diameter of $1\ \text{mm}$. If the resistivity of carbon is $3.5 \times 10^{-5}\ \Omega\ \text{m}$, what is the length of the wire?

[0.022 m]

- 6.

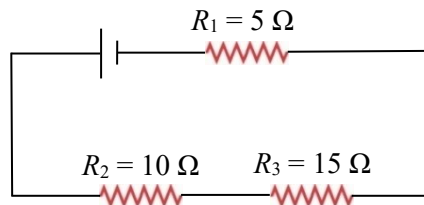


FIGURE 1

Three resistors, R_1 , R_2 and R_3 are connected to a battery as shown in **FIGURE 1**. Calculate the effective resistance of the circuit.

[30 Ω]

7.

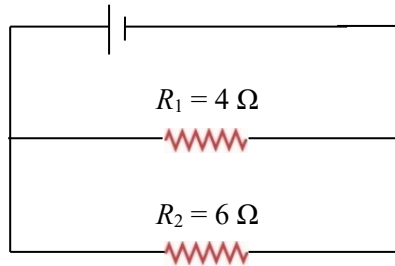


FIGURE 2

Two resistors, R_1 and R_2 are connected to a battery as shown in **FIGURE 2**. Calculate the effective resistance of the circuit.

[2.4 Ω]

8.

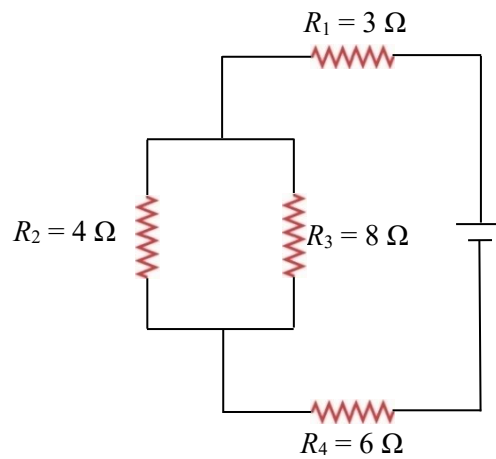


FIGURE 3

Based on **FIGURE 3**, calculate the effective resistance of the circuit.

[11.67 Ω]

9.

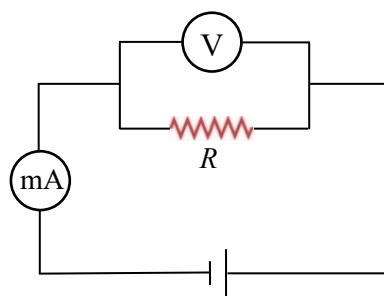


FIGURE 4

FIGURE 4 shows the electric circuit is used to determine the resistance of voltmeter. When the resistance R is 100 Ω , the reading of milliammeter is 30 mA and the reading of voltmeter is 2.7 V. Calculate the resistance of the voltmeter.

[900 Ω]

10.

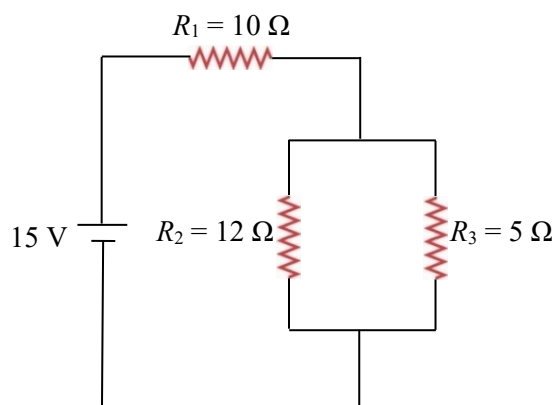


FIGURE 5

Three resistors R_1 , R_2 and R_3 are connected to a power supply of 15 V as shown in **FIGURE 5**. If the current that flows in R_1 is 1.11 A, calculate the

- (a) potential difference across resistor R_1 .
- (b) potential difference across resistor R_3 .

[11.1 V, 3.9 V]