

TOPIC 4 | REINFORCEMENT QUESTIONS DP024

Answer all the questions


- How much charge is on each plate of a $4.00\text{-}\mu\text{F}$ capacitor when it is connected to a 12.0-V battery?

[$48.0\mu\text{C}$]

- Two conductors having net charges of $+10.0\text{ }\mu\text{C}$ and $-10.0\text{ }\mu\text{C}$ have a potential difference of 10.0 V between them. Determine the capacitance of the system.


[$1.0\mu\text{F}$]

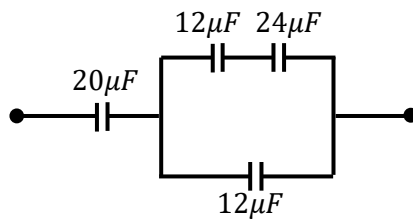- What is the equivalent capacitance of the combination shown?




[$10\mu\text{F}$]

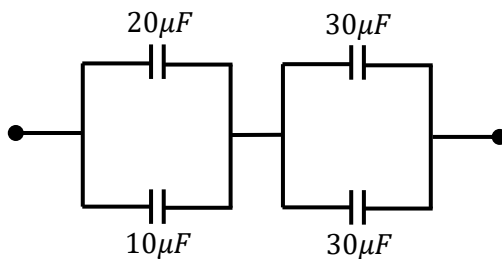- What is the equivalent capacitance of the combination shown?



[$20\mu\text{F}$]

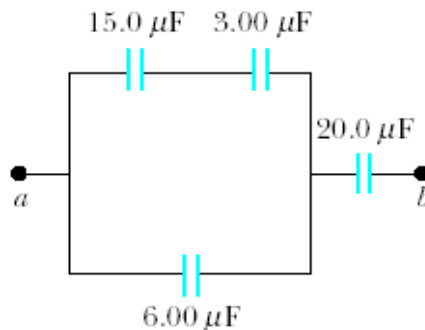
- Four capacitors are connected as shown in figure below. Find the equivalent capacitance between points a and b .



[$5.96\mu\text{F}$]

TOPIC 4 | REINFORCEMENT QUESTIONS DP024

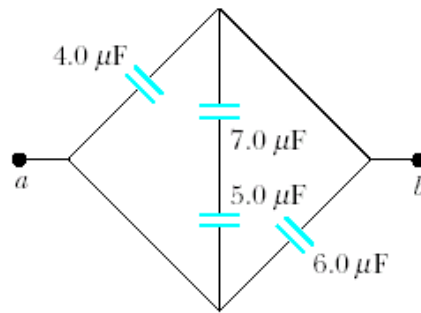6. Find the equivalent capacitance between points *a* and *b* in the combination of capacitors shown in Figure below.



[12.9 μF]

7. A $20\ \mu\text{F}$ capacitor has a charge of $240\ \mu\text{C}$ is connected to a $50\ \text{k}\Omega$ resistor. Calculate the time constant.

[1.0s]

8. Sketch and label the graph $Q - t$ of a capacitor during
- I. charging
 - II. discharging

9. A $12\ \mu\text{F}$ capacitor is charged to a potential difference of 6V . It is then disconnected and discharges through $20\ \text{k}\Omega$ resistor. Calculate
- I. The time constant
 - II. The charge remained in the capacitor after 0.5s .

[0.24s, $8.97 \times 10^{-6}\text{C}$]

10. A $1000\ \mu\text{F}$ capacitor is connected in series with a $2.0\ \text{k}\Omega$ resistor to a battery of 4.0V . Calculate the charge stored in the capacitor after 5.0s .

[$3.67 \times 10^{-3}\text{C}$]